

1 CIRCUIT ANALYSIS AND POWER CALCULATIONS

Consider the voltage and current waveforms taken from a single-phase circuit in Figure 1.


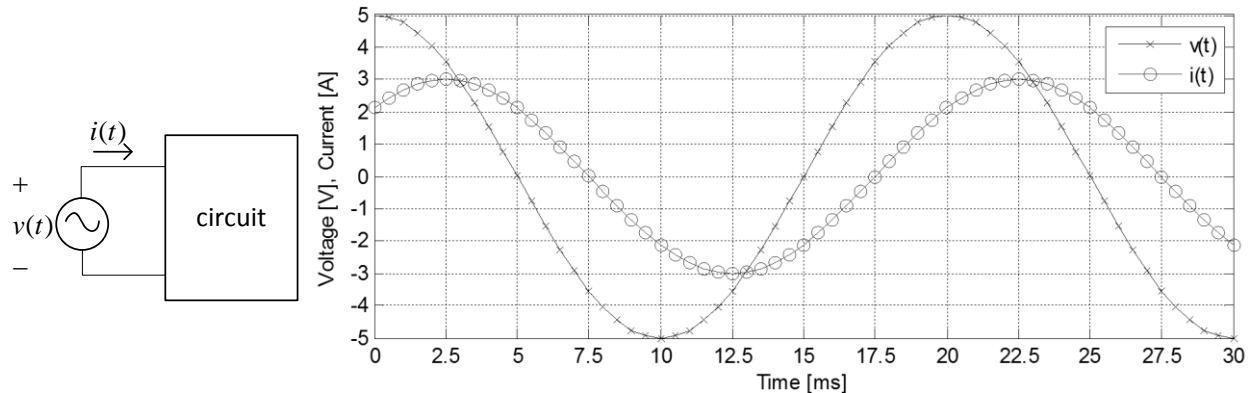


Figure 1: Single-phase circuit and time-domain waveforms of voltage and current

- Show that the phase angle difference between the voltage and current waveform is $\gamma = 45^\circ$
- Find an expression for the instantaneous power $p(t)$ **consumed** by the circuit. You don't need to simplify the expression.
- Find the active power P and the reactive power Q **consumed** by the circuit (*as usual, both P and Q should be average values*). Is the circuit capacitive or inductive? Explain why.
- Find the equivalent impedance Z_{eq} of the circuit.

2 STEP RESPONSES OF RC-CIRCUIT

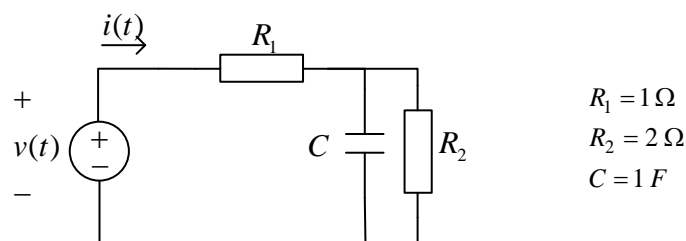Consider the following circuit and numerical values:



In problem a) and b) we assume that the voltage across the capacitor is zero at $t = 0$

- Show that the transfer function between $i(t)$ and $v(t)$ is $H(s) = \frac{V(s)}{I(s)} = \frac{2s+3}{2s+1}$

In problem b), we apply a voltage step at $t = 0$, i.e. $v(t) = \begin{cases} 0V & , t < 0 \\ 1V & , t \geq 0 \end{cases}$

- Based on the transfer function from a), find $i(t)$ for $t \geq 0$

In problem c) we assume that $v(t) = 100\cos(3t)$, and that the circuit has reached stationary/steady-state conditions.

- c) Since the circuit operates in stationary conditions the current can be written as $i(t) = A\cos(3t + \varphi)$. Find the numerical values for A [Ampere] and φ [radians].

3 MOTORS AND DRIVE SYSTEMS

Part 1: Induction motor

- a) Figure 2 shows a typical inductor motor curve relating the mechanical speed ω_{mek} to the mechanical torque T_{mek} . Disregard mechanical gear and magnetic poles. Redraw the curve into your answer, and indicate the following items in the figure:
- I. Synchronous speed ω_s
 - II. The speed at which the slip s equals 0.
 - III. The speed at which the slip s equals 1.
 - IV. The normal operating range
 - V. The starting torque T_{start}

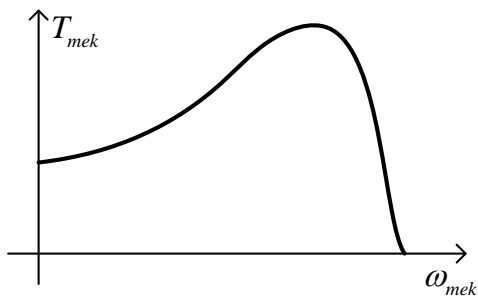


Figure 2: Induction motor mechanical torque versus mechanical speed

- b) What is the torque of the machine when the mechanical speed equals synchronous speed?

Part 2: Wind turbine system

A wind turbine generator is directly connected to a power grid with fixed frequency $f_{grid} = 50$ Hz as shown in Figure 3. The system does not have any mechanical gear, but the generator is equipped with an unknown number of poles. ω_{mek} is the mechanical speed of the turbine and generator.

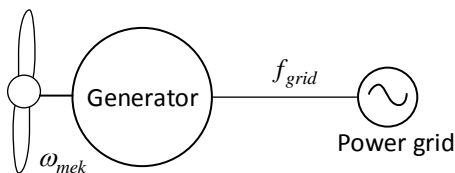


Figure 3: Wind turbine generator connected to a power grid

- c) Assume $\omega_{mek} = 7.85$ rad/s. How many poles is the generator equipped with?

In Figure 4 the relation between mechanical speed ω_{mek} and the produced power P_{wind} is presented for three different wind speeds $v = 6, 8, 10$ m/s.

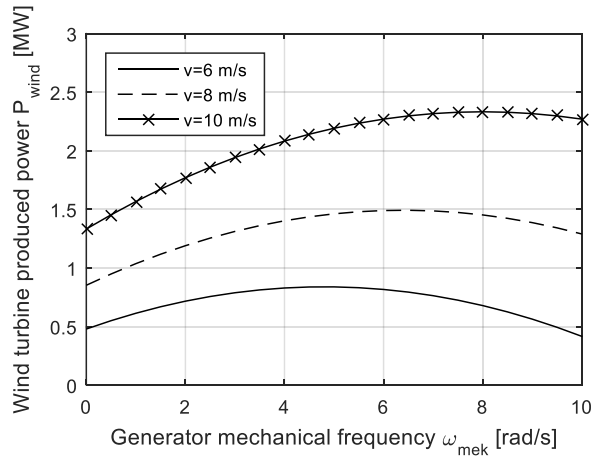


Figure 4: Relation between wind turbine mechanical speed ω_{mek} and produced power P_{wind}

- d) Assume $\omega_{mek} = 7.85$ rad/s and wind speed $v = 6$ m/s. Explain why the wind turbine configuration in Figure 3 is not optimal if the goal is to produce as much power as possible.
- e) Sketch a wind turbine configuration that is able to extract the maximum available power at every wind speed. What kind of converter configuration should be used?

4 DC-MOTOR CONTROLLED BY A DC-DC CONVERTER

Consider the DC-motor controlled by a DC-DC converter in Figure 5.

We can use the average voltage V_a when calculating torque and speed of the DC-motor by using the DC-motor formulas (appendix). The term *no-load* is defined as the condition where the machine is producing zero torque, i.e. $T = 0$

- a) Assume the average terminal voltage $V_a = 7.5$ V, and $R_a = 0.1 \Omega$. What is the no-load speed of the DC-motor when the flux constant is equal to $K\phi = 0.1 \frac{\text{rad}}{\text{s}} \cdot \frac{1}{\text{V}}$?

The DC-DC converter consists of an *ideal* switch S and an *ideal* diode D . The variable k is called *duty-cycle*: $k = \frac{t_{on}}{T_s}$, where t_{on} is the time period where the switch is closed (ON), and T_s is the period.

- b) Consider the waveform for $v_a(t)$ presented in Figure 6. Find the expression of the average

$$\text{voltage } V_a = \frac{1}{T_s} \int_0^{T_s} v_a(t) dt \text{ as a function of the duty-cycle } k \text{ and the DC-voltage } V_{dc}$$

NB: Note the difference between the duty cycle k and the flux constant K , and also the difference between torque T and period T_s

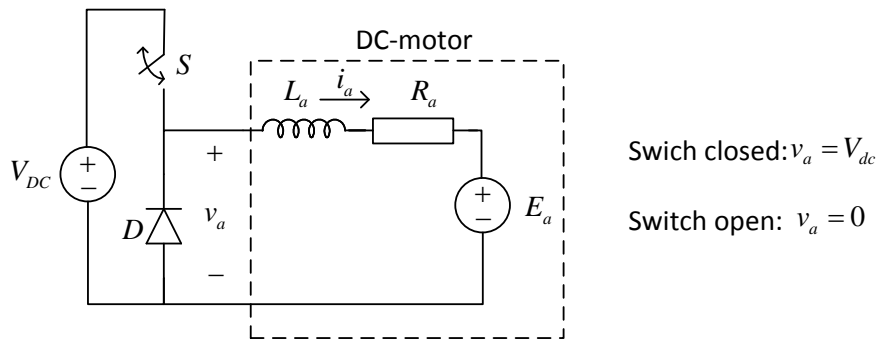


Figure 5: DC-motor controlled by a DC-DC converter

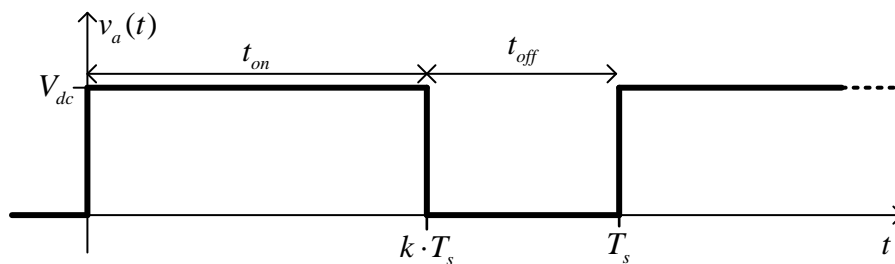


Figure 6: Waveform of the voltage applied to the DC-motor terminals (v_a)

- c) Draw the two separate circuit diagrams corresponding to *closed switch S* and *open switch S*. Indicate the path of current flow in the two diagrams. Finally, show that the differential equation for i_a can be written as:

$$\frac{di_a}{dt} = \begin{cases} \frac{V_{dc} - R_a i_a - E_a}{L_a}, & \text{ON-state (S is closed)} \\ \frac{-R_a i_a - E_a}{L_a}, & \text{OFF-state (S is open)} \end{cases}$$

Hint: Assume i_a is always positive, then the diode will always be on when the switch S is open.

Use the following numerical values in problem d):

$$V_{dc} = 15 \text{ V} \quad R_a = 0 \text{ } \Omega \quad L_a = 1 \text{ mH} \quad T_s = 2 \text{ ms} \quad k = 0.5 \quad E_a = 7.5 \text{ V}$$

- d) Assume $i_a(0) = 7.5 \text{ A}$. Calculate $i_a(t)$ for $0 \leq t \leq T_s$. Make a sketch of the waveform.

NB: Note that we have assumed $R_a = 0$ in order to simplify the calculations.

APPENDIX: FORMULAS

Inductor and capacitor

$$v_L = L \frac{di_L}{dt}, \quad i_C = C \frac{dv_C}{dt}, \quad X_L = j\omega L, \quad X_C = \frac{1}{j\omega C}$$

Phasors and complex power

$$X \cos(\omega t + \theta) \Leftrightarrow X e^{j\theta}, \quad S = VI^* = P + jQ$$

Electromagnetism:

$$\varepsilon = N \frac{d\varphi}{dt}, \quad NI = \Re \varphi, \quad \Re = \frac{l}{\mu A}, \quad \varphi = BA$$

Trigonometrics

$$\begin{aligned} \cos(2x) &= 1 - 2\sin^2(x) \\ &= 2\cos^2(x) - 1 \end{aligned}$$

$$\sin(2x) = 2\sin(x)\cos(x)$$

Three-phase

$$|V_{LL}| = \sqrt{3} |V_{ph}|$$

Electrical machines

$$f_{el} = \frac{P}{2} f_{mek}$$

DC-machine

$$E_a = K\varphi\omega \quad T = K\varphi I_a$$

Induction (asynchronous) machine

$$\omega_{mek} = (1-s)\omega_s$$

Mechanics

$$P = T\omega \quad P = F \cdot v \quad v = \omega r \quad E_k = \frac{1}{2}mv^2$$

Laplace transforms

$$\text{Konstant:} \quad \mathcal{L}(K \cdot f(t)) = K \cdot F(s)$$

$$\text{Sprangrespons:} \quad \mathcal{L}(u(t)) = \frac{1}{s}$$

$$\text{Eksponential:} \quad \mathcal{L}(e^{at}) = \frac{1}{s-a}$$

$$\text{s-shift:} \quad \mathcal{L}\{e^{-at} \cdot f(t)\} = F(s+a)$$

$$\text{Sinus:} \quad \mathcal{L}\{\sin(\omega t)\} = \frac{\omega}{s^2 + \omega^2}$$

$$\text{Cosinus:} \quad \mathcal{L}\{\cos(\omega t)\} = \frac{s}{s^2 + \omega^2}$$

$$\text{Dempa sinus:} \quad \mathcal{L}\{e^{-at} \sin(\omega t)\} = \frac{\omega}{(s+a)^2 + \omega^2}$$

$$\text{Dempa cosinus:} \quad \mathcal{L}\{e^{-at} \cos(\omega t)\} = \frac{s+a}{(s+a)^2 + \omega^2}$$