

# 1 DC MOTOR

The separately excited dc machine having the magnetization curve shown in Figure 1 is operating as a motor at a speed of 1500 rpm with a developed (shaft) power of 10 hp (1hp=735 Watt) and  $I_F = 2.5$  A. The armature resistance is  $R_A = 0.3 \Omega$  and the field resistance is  $R_F = 50 \Omega$ .

- Explain shortly why the magnetization curve in Figure 1 is curved at high field current. You can disregard this phenomenon in your subsequent calculations.
- Find the machine speed in radians per second
- In this operating condition, find the developed torque, the armature current  $I_A$  and the voltage  $V_T$  applied to the armature circuit.
- The field current is still  $I_F = 2.5$  A. Assume the terminal voltage is  $V_T = 127.5$  V and the power supplied to the motor terminals is 3.2 kW. What is the speed of the machine?

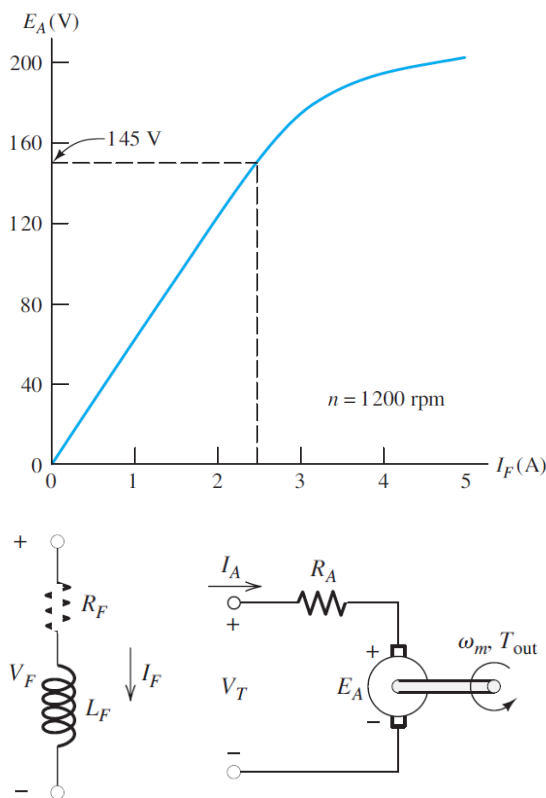


Figure 1: Magnetization curve for 200 V-10 hp dc motor and equivalent circuit of the dc machine

## 2 MAGNETIC CIRCUIT

For the core shown in Figure 2, the reluctances of all three paths between points *a* and *b* are equal.  $\mathfrak{R}_1 = \mathfrak{R}_2 = \mathfrak{R}_3 = 106 \text{ (A}\cdot\text{turns)/Wb}$  Assume that all of the flux is confined to the core.

- Do the fluxes produced by  $i_1$  and  $i_2$  aid or oppose one another in path 1? In path 2? In path 3? Explain why.
- If a dot is placed on the top end of coil 1, which end of coil 2 should carry a dot? Explain why. Make a simple sketch showing the dots.
- Should the mutual term for the voltages in the following equations carry a plus sign or a minus sign? Explain why

$$e_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt}$$

$$e_2 = \frac{d\lambda_2}{dt} = \pm M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

- Determine the values of  $L_1$ ,  $L_2$ , and  $M$ .

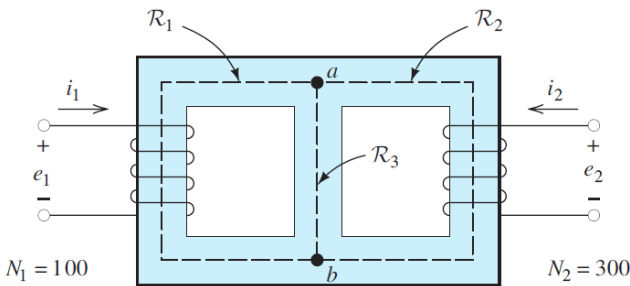


Figure 2: Magnetic circuit for problem 2

## 3 WIND TURBINE CONTROL AND GRID CONNECTION

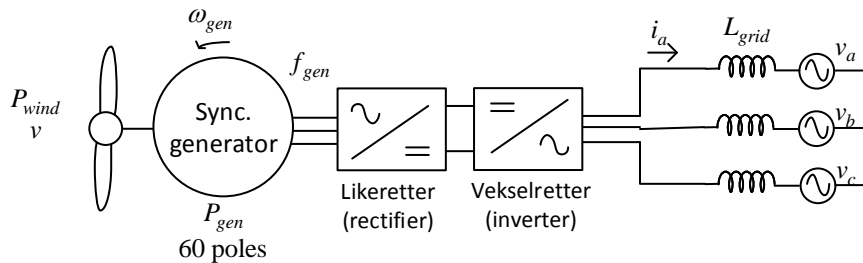


Figure 3: Overview of wind turbine with frequency converter

The wind turbine in Figure is connected to the grid by a generator, rectifier and inverter. The mechanical rotational speed of the generator is  $\omega_{gen}$ , while the electrical frequency of the generator voltages is  $f_{gen}$ . The maximum available power from the wind is  $P_{wind}$ , while the actually produced power is  $P_{gen}$ . The generator is a synchronous generator with 60 poles.

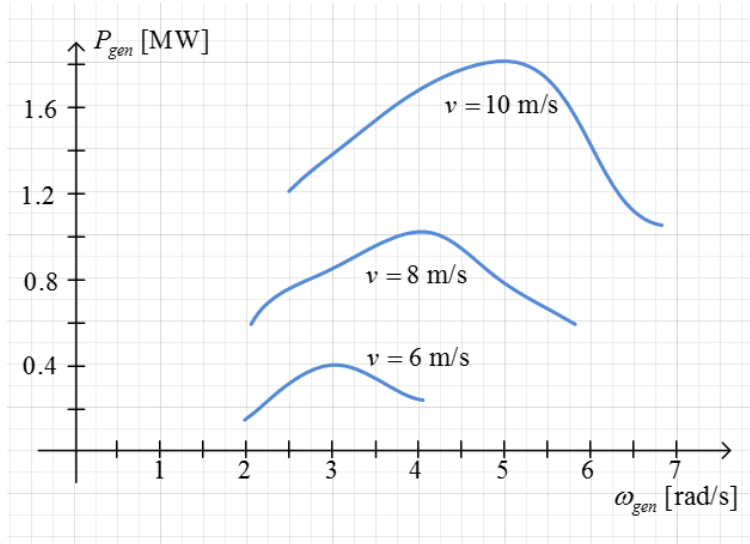


Figure 4: Wind power production curve as a function of generator speed (for three different wind speeds  $v$ )

The curves in Figure shows the wind power production  $P_{gen}$  as a function of generator mechanical speed  $\omega_{gen}$ .

- If the wind speed is 10 m/s, what is the produced power if the generator electrical frequency is  $f_{gen} = 18$  Hz?
- Use Figure to discuss the best strategy to control  $\omega_{gen}$ . Also, explain the concept of Maximum Power-Point Tracking (MPPT).

The maximum available power from the wind can be expressed by the formula  $P_{wind} = kv^3$ , where  $k$  is a constant and  $v$  is the wind speed. Assume  $k = 3480$ .

- Assume the turbine is controlled based on MPPT. What is the efficiency of the wind turbine for the three wind speeds in Figure? Efficiency is expressed as (produced power)/(available power).
- The turbine produces  $P_{gen} = 1.5$  MW. Neglect all losses in the generator, rectifier and inverter. The maximum allowed line current  $i_a$  is 350 A (RMS). Phase-to-phase grid voltage is 3000 V (RMS). What is the maximum possible reactive power that the inverter can supply to the grid? You can assume a symmetrical three-phase system, hence the per phase equivalent can be used.

## 4 PHASOR TRANSFORM

---

- a) Write the corresponding differential equations that models the RLC circuit in Figure 5. The source voltage is  $v(t) = V_0 \cos(\omega t + \alpha_v)$
- b) Transform the differential equations into phasor domain, keep in mind that  $\cos(\omega t + \theta) = \text{Re}(e^{j\theta} \cdot e^{j\omega t})$ ,  $\cos(\theta) = \text{Re}(e^{j\theta})$

Based on the analysis of the expression obtained in b) demonstrate the following:

- c) Demonstrate that the impedance of the series RLC circuit is  $Z = R + j(\omega L - \frac{1}{\omega C})$  and that the current phasor is  $I = \frac{V}{(R + j(\omega L - \frac{1}{\omega C}))}$
- d) Write the expression of the current in time domain,  $i(t)$ , as a function of the current phasor parameters found in part c)

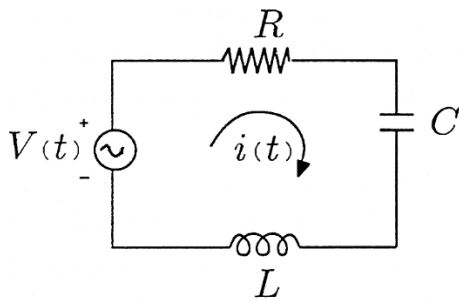


Figure 5: Series RLC circuit with  $v(t) = V_0 \cos(\omega t + \alpha_v)$

## APPENDIX: FORMULAS

---

### Inductance and capacitance

$$v_L = L \frac{di_L}{dt}, \quad i_C = C \frac{dv_C}{dt}, \quad X_L = \omega L, \quad X_C = \frac{1}{\omega C}$$

### Phasors and complex power

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$X \cos(\omega t + \theta) = \operatorname{Re}(X e^{j\theta} \cdot e^{j\omega t})$$

$$X \cos(\omega t + \theta) \xrightarrow{\text{Phasor Transform}} X e^{j\theta}, \quad S = VI^* = P + jQ$$

### Electromagnetism:

$$\varepsilon = N \frac{d\varphi}{dt}, \quad NI = \mathfrak{R}\varphi, \quad \mathfrak{R} = \frac{l}{\mu A}, \quad \varphi = BA$$

$$\lambda_1 = \lambda_{11} \pm \lambda_{12}$$

$$\lambda_2 = \pm \lambda_{21} + \lambda_{22}$$

$$L = \frac{N^2}{\mathfrak{R}}$$

$$L_1 = \frac{N_1 \varphi_1}{i_1}; \quad L_2 = \frac{N_2 \varphi_2}{i_2}$$

$$M = \frac{\lambda_{21}}{i_1} = \frac{\lambda_{12}}{i_2}$$

$$\lambda_1 = N_1 \varphi_1$$

$$\lambda_2 = N_2 \varphi_2$$

### Trigonometrics

$$\cos(2x) = 1 - 2\sin^2(x)$$

$$\sin(2x) = 2\sin(x)\cos(x)$$

### Three-phase

$$|V_{LL}| = \sqrt{3} |V_{ph}|$$

$$|S| = \sqrt{3} |V_{LL}| |I_L| = 3 |V_{ph}| |I_L|$$

$$|S| = \sqrt{P^2 + Q^2}$$

### Electrical machines

$$f_{el} = \frac{p}{2} f_{mech}$$

### DC-machine

$$E_A = K \varphi \omega_m \quad T_{out} = K \varphi I_A$$

$$\frac{E_{A1}}{E_{A2}} = \frac{n_1}{n_2} = \frac{\omega_1}{\omega_2}$$

### Inverters

$$\text{Single-phase: } m = \frac{\sqrt{2} |V_{ac}|}{V_{dc}}$$

$$\text{Three-phase: } m = \frac{2\sqrt{2} |V_{LL}|}{\sqrt{3} V_{dc}}$$

### Mechanics

$$P = T\omega \quad P = F \cdot v \quad v = \omega r \quad E_k = \frac{1}{2} m v^2$$

$$T_{mot} - T_{load} = J \frac{d\omega}{dt}$$

### Laplace transforms

$$\text{Constant: } \mathcal{L}(K \cdot f(t)) = K \cdot F(s)$$

$$\text{Step response: } \mathcal{L}(u(t)) = \frac{1}{s}$$

$$\text{Exponential: } \mathcal{L}(e^{at}) = \frac{1}{s-a}$$

$$\text{s-shift: } \mathcal{L}\{e^{-at} \cdot f(t)\} = F(s+a)$$

$$\text{Sine: } \mathcal{L}\{\sin(\omega t)\} = \frac{\omega}{s^2 + \omega^2}$$

$$\text{Cosine: } \mathcal{L}\{\cos(\omega t)\} = \frac{s}{s^2 + \omega^2}$$

$$\text{Damped cosine: } \mathcal{L}\{e^{-at} \cos(\omega t)\} = \frac{s+a}{(s+a)^2 + \omega^2}$$